


PROGRAMMING THE AD35 DC/DC CONVERTER

Referring to Figure 1A, amplifier A1 consists of a low voltage op amp and a high voltage NPN transistor Q1. By grounding the negative output of the AD35, the converter operates as a single positive output DC/DC from 0 to 200V.

A1 through Q1 sets the V_o ADJ voltage of AD35. At turn on, the $5V_{REF}$ of the converter through R3 will set the output to 200V if A1 is not powered up ($V_{CC} = V_{EE} = 0$). When V_{CC} and V_{EE} of A1 is turned on at the same time, the AD35 is turned on and A1 takes over the control of the output of AD35. A1 will wait for a few milliseconds due to the turn on delay and soft start of the AD35.

It must be pointed out that the AD35 operates as a non-inverting amplifier, i.e. V_{OUT} increases as V_o ADJ increases or, more specifically, V_o ADJ increases with respect to V_o COM. Therefore an inverting amplifier can be used to control the AD35. In this configuration,

the voltage gain of the linear block is given by the feedback resistor network R4 and R5. The linear block of A1 plus AD35 can be viewed as a single positive supply, adjustable amplifier that can be controlled through a positive input when V_{IN} is applied on the non-inverting input of A1 (the negative input of the op amp inside A1) or through a negative V_{IN} when the positive input of A1 is grounded through R6 and $-V_{IN}$ is applied at the open end of R5. As can be seen in Figure 1A, R1 and R2 are pull-down resistors to V_{EE} . Depending on the voltage used for V_{EE} , select R2 such that V_c of Q1 is a few millivolts (mV) negative when $V_o = 0V$ and Q1 is at saturation. The collector current of Q1 is the current through R3 required to set V_o ADJ to 0V.

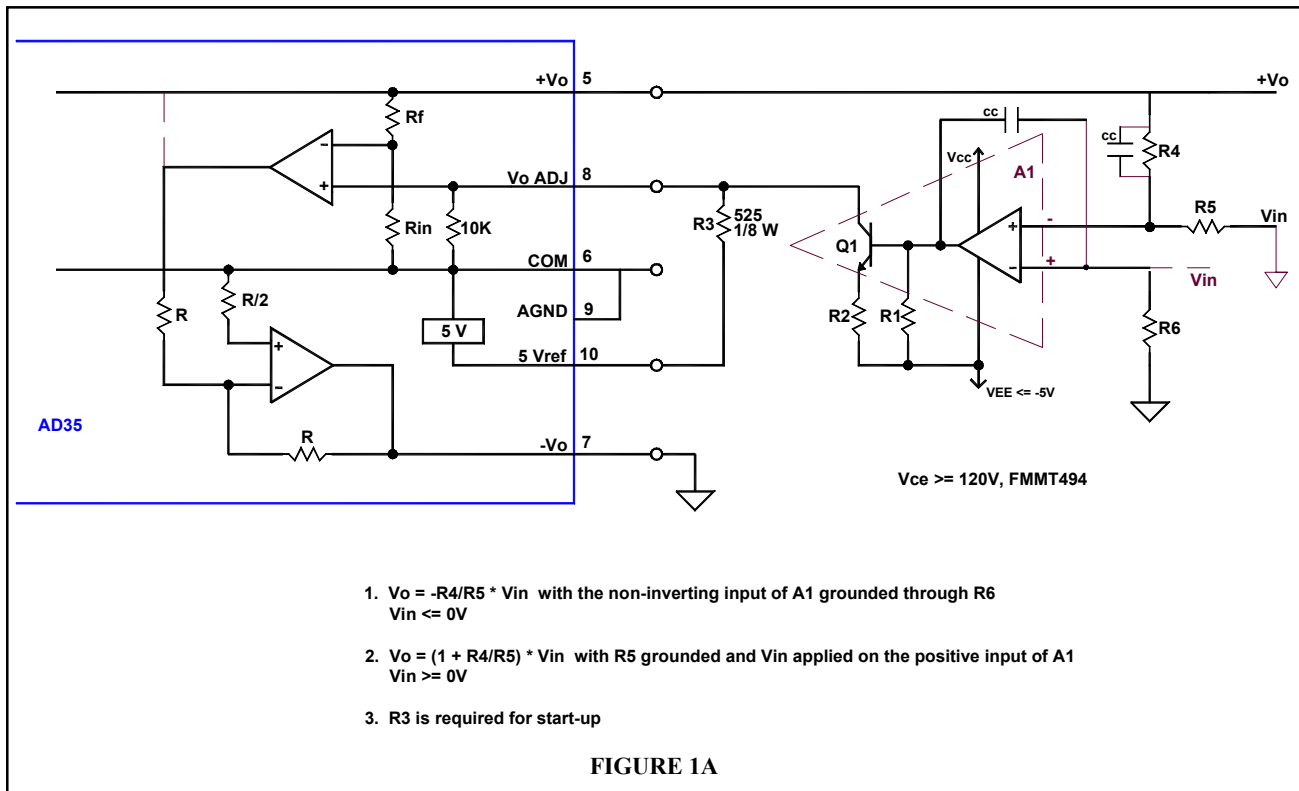

$$5V/R3 = I \leq 9.5mA$$

and


$$V_{CE} + I \cdot R^2 = V_{EE}$$

For V_{CE} of Q1 = 100mV, $V_{EE} = -5V$, $I = 9.6mA$

$$R2 = (5 - 0.1)/9.6 = 510\Omega$$

R1 is required only if the output voltage of the selected amplifier inside A1 cannot go rail to rail such as LM358, MC34072 and others. R1 will pull the output to V_{EE} forcing Q1 off and the collector current to zero when $+V_o$ is set for the V_o maximum of 200V.

A photo coupler can also be used as the output stage of A1 to replace Q1 (see Figure 1B). The collector of the phototransistor is connected to V_o ADJ (Pin 8 of AD35) while the photodiode will be connected as is to the emitter of Q1 (between R2 cathode and the output of the OPAM inside A1 anode). The accuracy of the linear block depends only on the accuracy of V_{IN} and its feedback network R4 and R5.

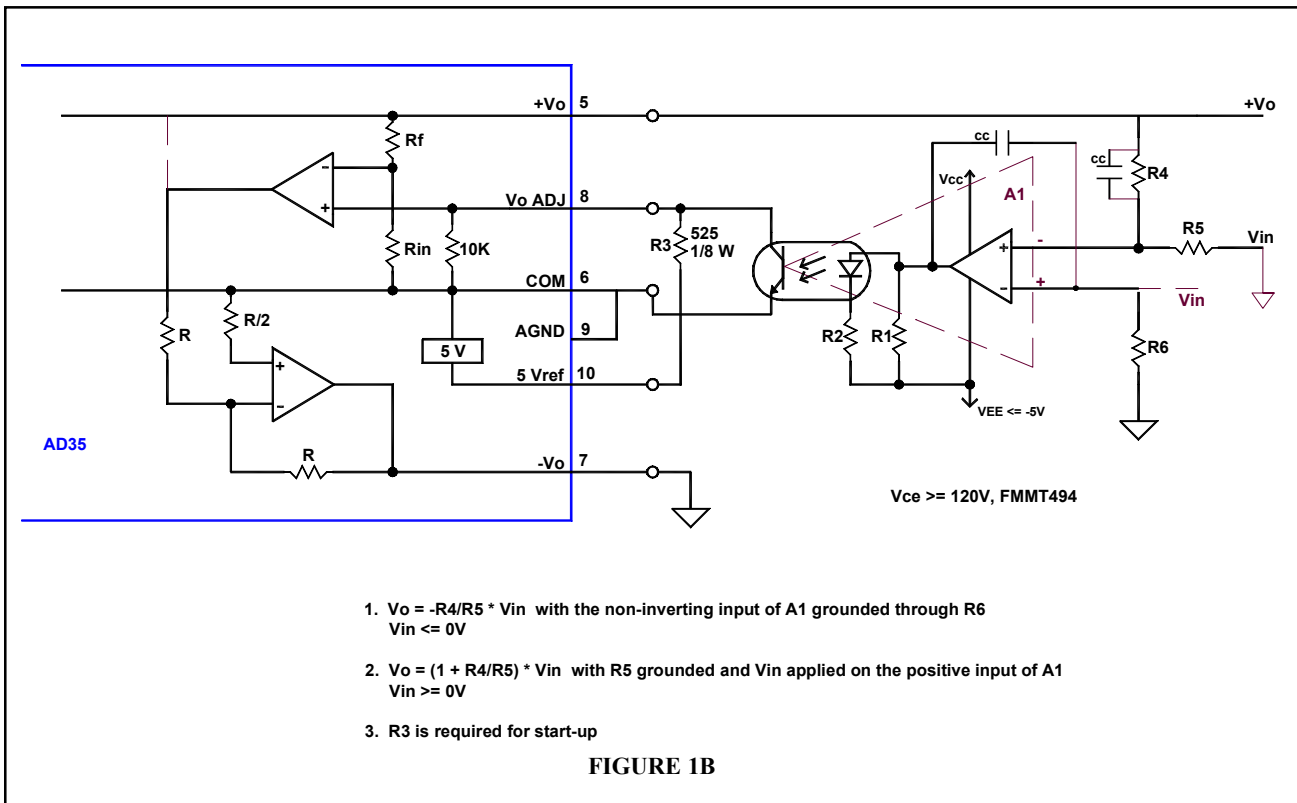

Referring to Figure 4, the AD35 is connected for a negative output. The current source consists of A1, a P-channel high-voltage MOSFET and a stable voltage source V_x . From the data sheet, V_o is given by:

#1 $V_o = 42 * V_o \text{ ADJ}$

#2 $V_o \text{ ADJ} = 10 * I$ or $(10 || R_x) * I$ if R_x is installed

$$I = (V_x - V_{D/A}) / R_{CS}$$

If an open circuit protection is needed, the same approach used in Figure 2 will force $V_{D/A}$ to V_x , thus the current through R_{CS} will be zero.

